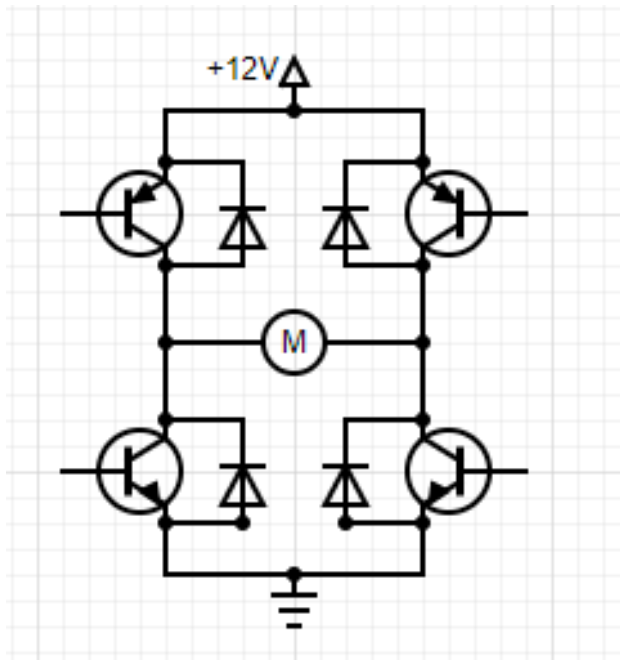


H-Bridge

Circuit:



Transistors:

- Two TIP120 npn Transistors.
- Two TIP125 pnp Transistors.

*This H-Bridge can handle up to 5 amps.